

# 电子学基础——第十二次作业

LXQ

2019.12.26

**12.1** Determine the transfer function,  $Y/X$ , for the systems shown in Fig. 12-77.

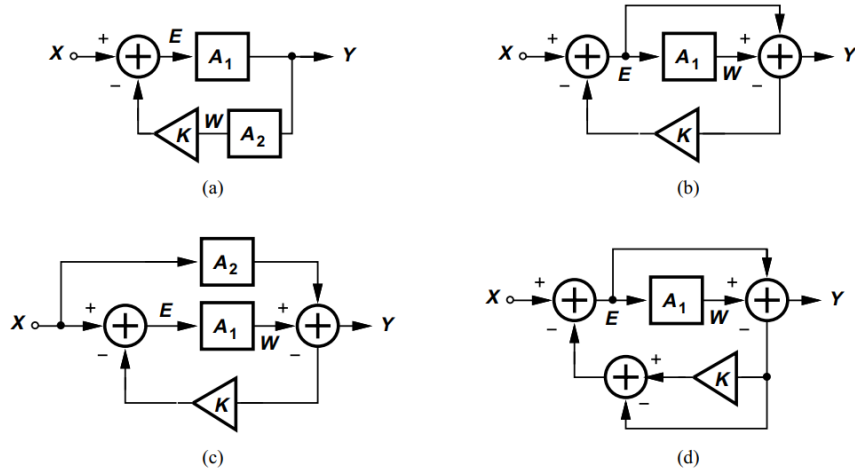


Figure 12-77

解 (a)

$$\begin{cases} E = X - EA_1A_2K \\ Y = EA_1 \end{cases}$$

$$\therefore \frac{Y}{X} = \frac{A_1}{1 + A_1A_2K}$$

(b)

$$\begin{cases} E = X - (EA_1 - E)K \\ Y = EA_1 - E \end{cases}$$

$$\therefore \frac{Y}{X} = \frac{A_1 - 1}{1 + (A_1 - 1)K}$$

(c)

$$\begin{cases} E = X - (EA_1 - A_2X)K \\ Y = EA_1 - A_2X \end{cases}$$

$$\therefore \frac{Y}{X} = \frac{A_1 - A_2}{1 + A_1K}$$

(d)

$$\begin{cases} E = X - [(EA_1 - E)K - (EA_1 - E)] \\ Y = EA_1 - E \end{cases}$$

$$\therefore \frac{Y}{X} = \frac{A_1 - 1}{1 + (K - 1)(A_1 - 1)}$$

**12.4** Calculate the loop gain of the circuits illustrated in Fig. 12-78. Assume the op amp exhibits an open-loop gain of  $A_1$ , but is otherwise ideal. Also  $\lambda = 0$ .

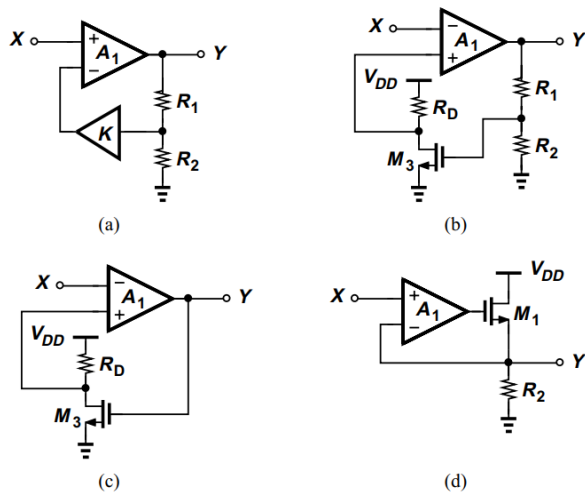


Figure 12-78

解 (a) 如图 p12-4-a, 在  $A_1$  输出端断开环路。

$$v_N = \frac{-R_2 v_t K A_1}{R_1 + R_2}$$

则环路增益为  $\frac{R_2 K A_1}{R_1 + R_2}$

(b) 如图 p12-4-b, 在  $A_1$  输出端断开环路。

$$v_N = \frac{-R_2 v_t g_{m3} R_D A_1}{R_1 + R_2}$$

则环路增益为  $\frac{R_2 g_{m3} R_D A_1}{R_1 + R_2}$

(c) 如图 p12-4-c, 在  $A_1$  输出端断开环路。

$$v_N = -v_t g_{m3} R_D A_1$$

则环路增益为  $g_{m3} R_D A_1$

(d) 如图 p12-4-d, 在  $A_1$  反相输入端断开环路。

$$v_N = -v_t A_1 \cdot \frac{g_{m1} R_2}{1 + g_{m1} R_2}$$

则环路增益为  $A_1 \cdot \frac{g_{m1} R_2}{1 + g_{m1} R_2} \approx A_1$

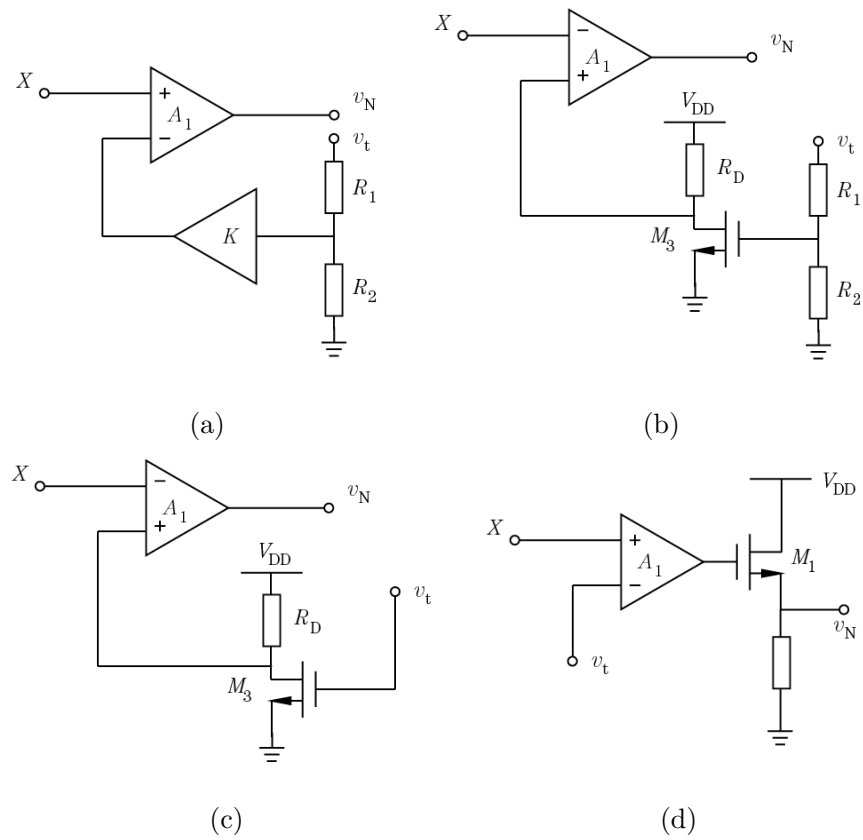


Figure p12-4

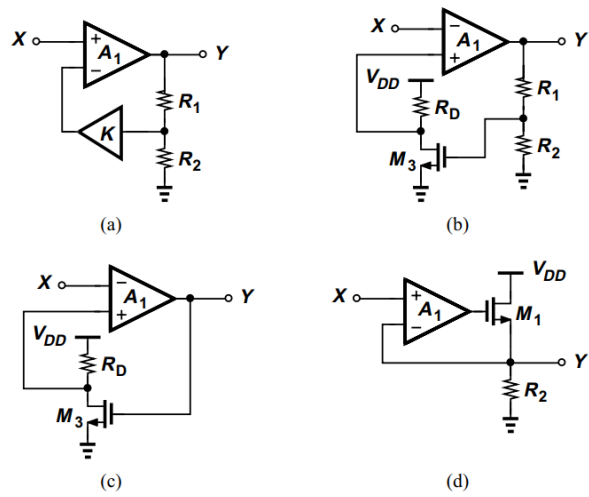


Figure 12-78

**12.5** Using the results obtained in Problem 12.4, compute the closed-loop gain of the circuits shown in Fig. 12-78.

解 (a)

$$A_{v,close} = \frac{A_1}{1 + \frac{R_2 K A_1}{R_1 + R_2}}$$

(b)

$$A_{v,close} = \frac{-A_1}{1 + \frac{R_2 g_{m3} R_D A_1}{R_1 + R_2}}$$

(c)

$$A_{v,close} = \frac{-A_1}{1 + g_{m3} R_D A_1}$$

(d)

$$A_{v,close} = \frac{-A_1 g_{m1} R_2}{1 + A_1 \cdot \frac{g_{m1} R_2}{1 + g_{m1} R_2}} \approx \frac{-A_1 g_{m1} R_2}{1 + A_1}$$

**12.10** The circuit of Fig. 12-80 must achieve a closed-loop  $-3\text{dB}$  bandwidth of  $B$ . Determine the required value of  $K$ . Neglect other capacitances and assume  $\lambda > 0$ .

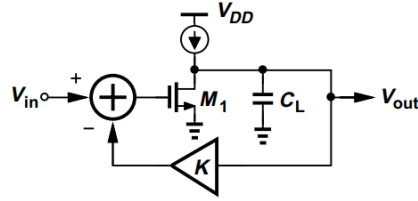


Figure 12-80

解

$$\omega_0 = \frac{1}{C_L r_{o1}}$$

$$A_0 = -g_{m1} r_{o1}$$

$$B = (1 + |A_0|K)\omega_0$$

$$\therefore K = \frac{C_L r_{o1} B - 1}{g_{m1} r_{o1}}$$

**12.22** Determine the polarity of feedback in each of the stages illustrated in Fig. 12-87.

解 (a) 设  $M_1$  栅端电压  $V_1$  上升, 由  $M_1$  栅漏反极性可知  $V_{out}$  下降, 又由  $M_2$  栅源同极性知  $V_1$  下降, 从而为负反馈。

(b) 设  $M_1$  栅端电压  $V_1$  上升, 由  $M_1$  栅漏反极性可知  $V_{out}$  下降, 又由  $M_2$  栅漏反极性知  $V_1$  上升, 从而为正反馈。

(c) 设  $M_1$  栅端电压  $V_1$  上升, 由  $M_1$  栅漏反极性可知  $V_{out}$  下降, 又由  $M_2$  源漏同极性知  $V_1$  下降, 从而为负反馈。

(d) 设  $M_1$  源端电压  $V_1$  上升, 由  $M_1$  源漏同极性可知  $V_{out}$  上升, 又由  $M_2$  栅漏反极性知  $V_1$  下降, 从而为负反馈。

**12.25** Consider the feedback circuit shown in Fig. 12-88, where  $R_1 + R_2 \gg R_D$ . Compute the closed-loop gain and I/O impedances of the circuit. Assume  $\lambda \neq 0$ .

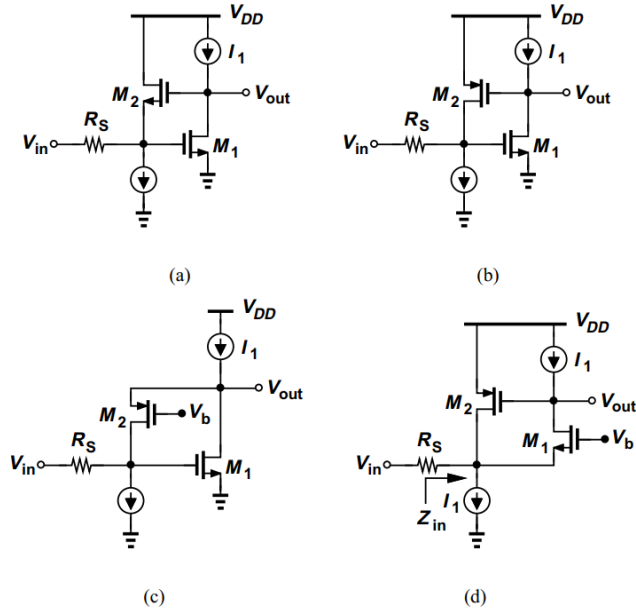


Figure 12-87

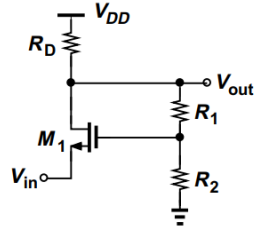


Figure 12-88

解

$$\begin{aligned}
 A_0 &= g_{m1}[R_D/(R_1 + R_2)/r_{o1}] \approx g_{m1}(R_D/r_{o1}) \\
 K &= \frac{R_2}{R_1 + R_2} \\
 R_{in} &= \frac{1}{g_{m1}} \\
 R_{out} &= R_D/(R_1 + R_2)/r_{o1} \approx R_D/r_{o1}
 \end{aligned}$$

$$\begin{aligned}
 \therefore A_{v,close} &= \frac{g_{m1}(R_D/r_{o1})}{1 + \frac{g_{m1}(R_D/r_{o1})R_2}{R_1 + R_2}} \\
 R_{in,close} &= \frac{1}{g_{m1}} \left[ 1 + \frac{g_{m1}(R_D/r_{o1})R_2}{R_1 + R_2} \right] \\
 R_{out,close} &= \frac{R_D/r_{o1}}{1 + \frac{g_{m1}(R_D/r_{o1})R_2}{R_1 + R_2}}
 \end{aligned}$$

**12.33** The amplifier depicted in Fig. 12-95 consists of a common-gate stage ( $M_1$  and  $R_D$ ) and a feedback network ( $R_1$ ,  $R_2$  and  $M_2$ ). Assuming  $R_1 + R_2$  is very large and  $\lambda = 0$ , compute the closed-loop gain and I/O impedances.

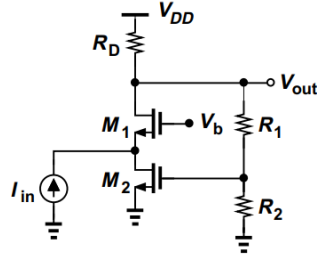


Figure 12-95

解

$$R_0 = \frac{1}{g_{m1}} \cdot g_{m1} [R_D // (R_1 + R_2)] \approx R_D$$

$$K = \frac{R_2 g_{m2}}{R_1 + R_2}$$

$$R_{in} = \frac{1}{g_{m1}}$$

$$R_{out} = R_D // (R_1 + R_2) \approx R_D$$

$$\therefore R_{v,close} = \frac{R_D}{1 + \frac{R_D R_2 g_{m2}}{R_1 + R_2}}$$

$$R_{in,close} = \frac{1}{g_{m1} \left( 1 + \frac{R_D R_2 g_{m2}}{R_1 + R_2} \right)}$$

$$R_{out,close} = \frac{R_D}{1 + \frac{R_D R_2 g_{m2}}{R_1 + R_2}}$$

**12.56** Compute the closed-loop gain and I/O impedances of the stages illustrated in Fig. 12-117.

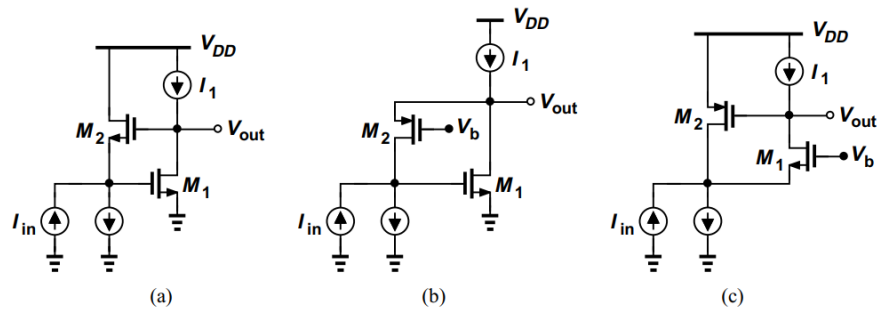


Figure 12-117

解 (a) 视 $M_2$ 为反馈部分。

$$\begin{aligned}
 R_{in} &= \frac{1}{g_{m2}} \\
 R_{out} &= r_{o1} // r_{o2} \\
 R_0 &= -\frac{g_{m1}}{g_{m2}}(r_{o1} // r_{o2}) \\
 K &= g_{m2} \cdot \frac{g_{m2}r_{o2}}{1 + g_{m2}r_{o2}} \approx g_{m2} \\
 \therefore R_{v,close} &= \frac{-\frac{g_{m1}}{g_{m2}}(r_{o1} // r_{o2})}{1 + g_{m1}(r_{o1} // r_{o2})} \\
 R_{in,close} &= \frac{1}{g_{m2}[1 + g_{m1}(r_{o1} // r_{o2})]} \\
 R_{out,close} &= \frac{r_{o1} // r_{o2}}{1 + g_{m1}(r_{o1} // r_{o2})}
 \end{aligned}$$

(b) 视 $M_2$ 为反馈部分。

$$\begin{aligned}
 R_{in} &= r_{o2} \\
 R_{out} &= r_{o1} // \frac{1}{g_{m2}} \approx \frac{1}{g_{m2}} \\
 R_0 &= -r_{o1}g_{m1}\left(\frac{1}{g_{m2}} // r_{o1}\right) \approx -\frac{r_{o2}g_{m1}}{g_{m2}} \\
 K &= g_{m2}
 \end{aligned}$$

$$\begin{aligned}
 \therefore R_{v,close} &= \frac{-r_{o2}g_{m1}}{g_{m2}(1 + g_{m1}r_{o2})} \\
 R_{in,close} &= \frac{r_{o2}}{1 + g_{m1}r_{o2}} \\
 R_{out,close} &= \frac{1}{g_{m2}(1 + g_{m1}r_{o2})}
 \end{aligned}$$

(c) 视 $M_2$ 为反馈部分。

$$\begin{aligned}
 R_{in} &= r_{o2} // \frac{1}{g_{m1}} \approx \frac{1}{g_{m1}} \\
 R_{out} &= r_{o1} \\
 R_0 &= \frac{1}{g_{m1}} \cdot g_{m1}r_{o1} = r_{o1} \\
 K &= -\frac{1}{g_{m1}} \cdot g_{m2}g_{m1} = -g_{m2} \\
 \therefore R_{v,close} &= \frac{r_{o1}}{1 + r_{o1}g_{m2}} \\
 R_{in,close} &= \frac{1}{(1 + r_{o1}g_{m2})g_{m1}} \\
 R_{out,close} &= \frac{r_{o1}}{1 + r_{o1}g_{m2}}
 \end{aligned}$$