

# 电子学基础——第十次作业

计83 刘轩奇 2018011025

2019.12.12

**8.10** A truck weighing station incorporates a sensor whose resistance varies linearly with the weight:  $R_S = R_0 + \alpha W$ . Here  $R_0$  is a constant value,  $\alpha$  a proportionality factor, and  $W$  the weight of each truck. Suppose  $R_S$  plays the role of  $R_2$  in the noninverting amplifier (Fig. 8-47). Also,  $V_{in} = 1V$ . Determine the gain of the system, defined as the change in  $V_{out}$  divided by the change in  $W$ .

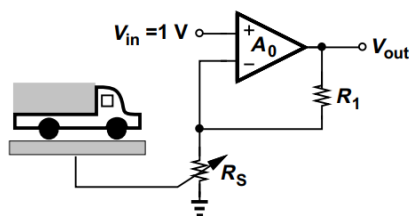


Figure 8-47

解

$$\begin{aligned}
 V_- &= V_+ = 1V \\
 \therefore V_{out} &= V_+ + \frac{V_-}{R_S} \cdot R_1 = \left(1 + \frac{R_1}{R_S}\right)V_{in} \\
 \therefore V_{out} &= \left(1 + \frac{R_1}{R_0 + \alpha W}\right)V_{in} \\
 \therefore \frac{\partial V_{out}}{\partial W} &= \frac{-\alpha R_1 V_{in}}{(R_0 + \alpha W)^2} = \frac{-\alpha R_1}{(R_0 + \alpha W)^2}
 \end{aligned}$$

**8.17** An inverting amplifier is designed for a nominal gain of 8 and a gain error of 0.1% using an op amp that exhibits an output impedance of  $2k\Omega$ . If the input impedance of the circuit must be equal to approximately  $1k\Omega$ , calculate the required open-loop gain of the op amp.

解

$$\begin{cases} \frac{R_F}{R_{in}} = 8 \\ \frac{1}{A_0} \left(1 + \frac{R_F}{R_{in}}\right) = 0.1\% \end{cases}$$

$$\therefore A_0 = 9000$$

**8.19** The integrator of Fig. 8-51 senses an input signal given by  $V_{in} = V_0 \sin \omega t$ . Determine the output signal amplitude if  $A_0 = \infty$ .

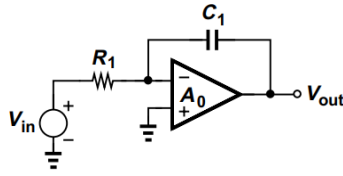


Figure 8-51

解

$$\dot{V}_{out} = -\frac{j}{\omega C_1 R_1} \dot{V}_{in}$$

则  $V_{out}$  振幅为  $\frac{V_0}{\omega C_1 R_1}$

**8.24** The differentiator of Fig. 8-52 is used to amplify a sinusoidal input at a frequency of 1MHz by a factor of 5. If  $A_0 = \infty$ , determine the value of  $R_1 C_1$ .

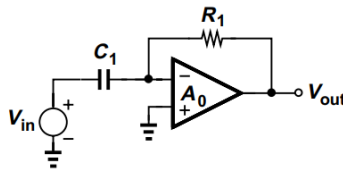


Figure 8-52

解

$$\dot{V}_{out} = jR_1 C_1 \omega \dot{V}_{in}$$

$$\therefore R_1 C_1 \omega = 5, R_1 C_1 = 7.96 \times 10^{-7} \text{s/rad}^{-1}$$

**8.32** The voltage adder of Fig. 8-54 employs an op amp having a finite output impedance,  $R_{out}$ . Using the op amp model depicted in Fig. 8-44, compute  $V_{out}$  in terms of  $V_1$  and  $V_2$ .

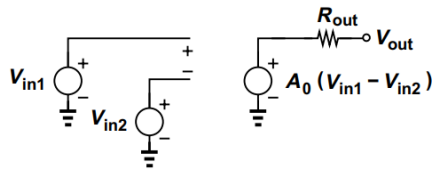


Figure 8-44

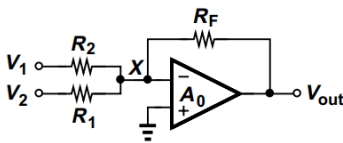


Figure 8-54

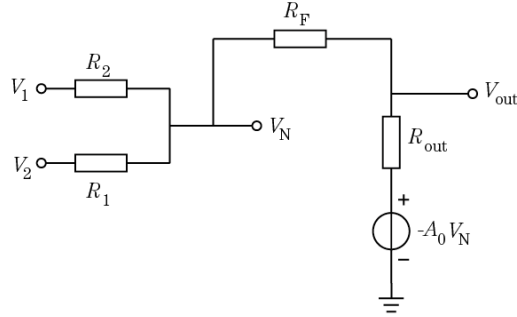


Figure p8-32

解 等效电路如图 p8-32 所示。

$$\begin{cases} V_{out} = V_N - R_F \left( \frac{V_1 - V_N}{R_2} + \frac{V_2 - V_N}{R_1} \right) \\ \frac{V_N + A_0 V_N}{R_F + R_{out}} = \frac{V_1 - V_N}{R_2} + \frac{V_2 - V_N}{R_1} \end{cases}$$

$$\therefore V_{out} = \frac{(R_1 V_1 + R_2 V_2) \left[ 1 - \frac{R_F(1+A_0)}{R_F + R_{out}} \right]}{R_1 + R_2 + \frac{R_1 R_2 (1+A_0)}{R_F + R_{out}}}$$

**8.33** Due to a manufacturing error, a parasitic resistance  $R_P$  has appeared in the adder of Fig. 8-55. Calculate  $V_{out}$  in terms of  $V_1$  and  $V_2$  for  $A_0 = \infty$  and  $A_0 < \infty$ . (Note that  $R_P$  can also represent the input impedance of the op amp.)

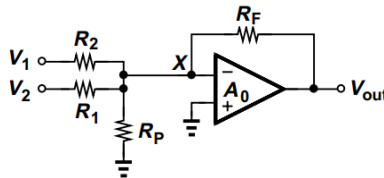


Figure 8-55

解 等效电路如图 p8-33 所示。

$$\begin{cases} I = \frac{V_N + A_0 V_N}{R_F + R_{out}} \\ I = \frac{V_1 - V_N}{R_2} + \frac{V_2 - V_N}{R_1} - \frac{V_N}{R_P} \\ V_{out} = V_N - R_F I \end{cases}$$

$$\therefore V_{out} = \left[ 1 - \frac{R_F(1+A_0)}{R_F + R_{out}} \right] \frac{\frac{V_1}{R_2} + \frac{V_2}{R_1}}{\frac{1}{R_2} + \frac{1}{R_1} + \frac{1}{R_P} + \frac{1+A_0}{R_F + R_{out}}}$$

$$R_{out} \rightarrow +\infty, V_{out} \rightarrow \frac{\frac{V_1}{R_2} + \frac{V_2}{R_1}}{\frac{1}{R_2} + \frac{1}{R_1} + \frac{1}{R_P}}$$

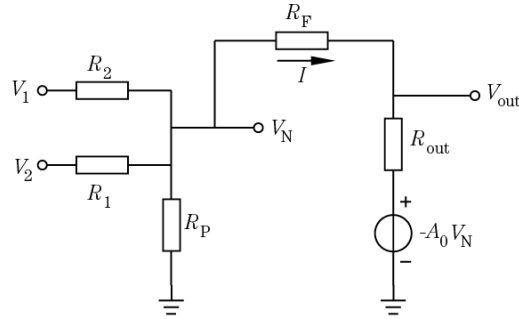


Figure p8-33

**8.34** Consider the voltage adder illustrated in Fig. 8-56, where  $R_P$  is a parasitic resistance and the op amp exhibits a finite input impedance. With the aid of the op amp model shown in Fig. 8-44, determine  $V_{out}$  in terms of  $V_1$  and  $V_2$ .

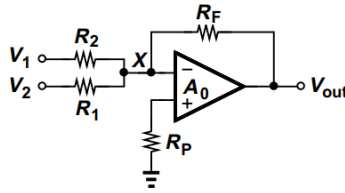


Figure 8-56

**解** 等效电路如图 p8-34 所示。由于  $V_P$  处无电流，则  $V_P = 0$ ，从而可以忽略  $R_P$  的影响，则答案同题 8.32:

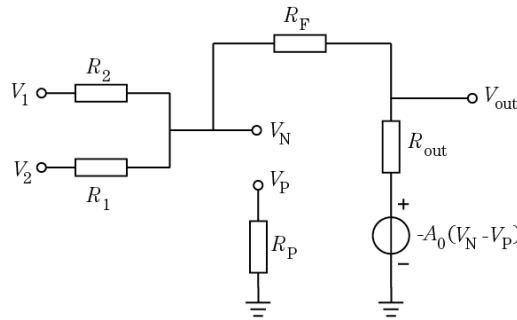


Figure p8-34

$$V_{out} = \frac{(R_1 V_1 + R_2 V_2) \left[ 1 - \frac{R_F(1+A_0)}{R_F + R_{out}} \right]}{R_1 + R_2 + \frac{R_1 R_2(1+A_0)}{R_F + R_{out}}}$$

$$R_{out} \rightarrow +\infty, V_{out} \rightarrow \frac{R_1 V_1 + R_2 V_2}{R_1 + R_2}$$

**8.46** Calculate  $V_{out}$  in terms of  $V_{in}$  for the circuit shown in Fig. 8-61.

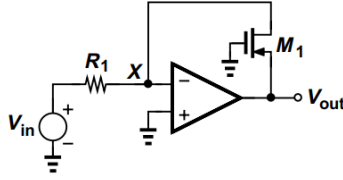


Figure 8-61

解 对  $M_1$ ,  $V_D = 0$ ,  $I_D = \frac{V_{in}}{R_1}$ , 又

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (-V_{out} - V_{th})^2$$

$$\therefore V_{out} = \sqrt{\frac{2V_{in}}{R_1 \mu_n C_{ox} (\frac{W}{L})}} - V_{th}$$

**9.50** Determine the value of  $R_P$  in the circuit of Fig. 9-70 such that  $I_1 = 2I_{REF}$ . With this choice of  $R_P$ , does  $I_1$  change if the threshold voltage of both transistors increases by  $\Delta V$ ?

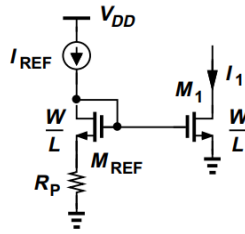


Figure 9-70

解  $M_{REF}$  可视为  $\frac{1}{g_{mREF}}$  电阻, 源端电压  $V_S = I_{REF} R_P$ , 漏端电压同栅端电压  $V_D = V_G = I_{REF} (\frac{1}{g_{mREF}} + R_P)$

$$\begin{cases} I_{REF} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (I_{REF} \frac{1}{g_{mREF}} - V_{th})^2 \\ I_1 = 2I_{REF} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (I_{REF} (\frac{1}{g_{mREF}} + R_P) - V_{th})^2 \end{cases}$$

$$\therefore R_P = (\sqrt{2} - 1) (\frac{1}{g_{mREF}} - \frac{V_{th}}{I_{REF}})$$

当确定  $R_P$ ,  $V_{th}$  增长到  $V'_{th} = V_{th} + \Delta V$  时,

$$\frac{I_1}{I_{REF}} = \left( \frac{I_{REF} (\frac{1}{g_{mREF}} + R_P)}{I_{REF} \frac{1}{g_{mREF}}} \right)^2$$

$$\frac{dI_1}{dV_{th}} (R_P) = 2I_{REF} \frac{I_{REF} (\frac{1}{g_{mREF}} + R_P)}{I_{REF} \frac{1}{g_{mREF}}} \cdot \frac{I_{REF} R_P}{(I_{REF} \frac{1}{g_{mREF}} - V_{th})^2}$$

$$= 2\sqrt{2} I_{REF} \frac{I_{REF} R_P}{(I_{REF} \frac{1}{g_{mREF}} - V_{th})^2}$$

$$= \frac{(4 - 2\sqrt{2}) I_{REF}}{I_{REF} \frac{1}{g_{mREF}} - V_{th}}$$

$$\therefore \Delta I_1 = \frac{(4 - 2\sqrt{2})I_{REF}}{I_{REF} \frac{1}{g_{mREF}} - V_{th}} \Delta V$$

**9.52** Calculate  $I_{copy}$  in each of the circuits shown in Fig. 9-71. Assume all of the transistors operate in saturation.

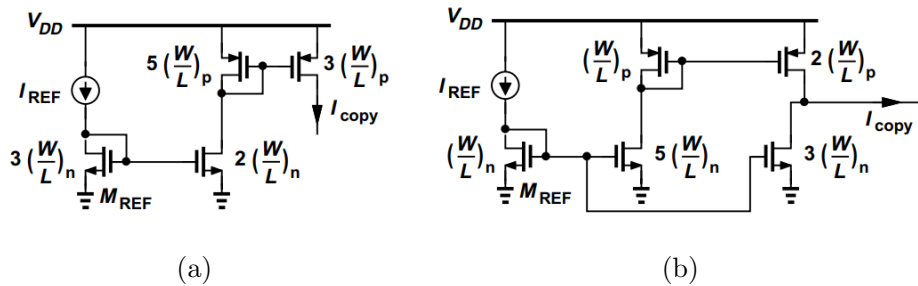


Figure 9-71

**解** 以下各电流符号中下标表示长宽比所对应的MOS管的电流。

(a)  $I_{2n} = \frac{2}{3}I_{REF}, I_{copy} = \frac{2}{3} \cdot \frac{3}{5} \cdot I_{REF} = \frac{2}{5}I_{REF}$

(b)  $I_{5n} = 5I_{REF}, I_{2p} = 10I_{REF}, I_{3p} = 3I_{REF}$

$$\therefore I_{copy} = 7I_{REF}$$