

电子学基础——第九次作业

计83 刘轩奇 2018011025

2019.12.05

10.51 A student who has a single-ended voltage source constructs the circuit shown in Fig. 10-75, hoping to obtain differential outputs. Assume perfect symmetry but $\lambda = 0$ for simplicity.

(b) Viewing M_1 as a common-source stage degenerated by the impedance seen at the source of M_2 , calculate v_X in terms of v_{in} .

(b) Viewing M_1 as a source follower and M_2 as a common-gate stage, calculate v_Y in terms of v_{in} .

(c) Add the results obtained in (a) and (b) with proper polarities. If the voltage gain is defined as $(v_X - v_Y)/v_{in}$, how does it compare with the gain of differentially driven pairs?

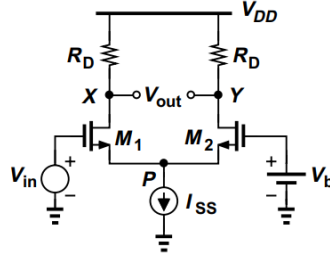


Figure 10-75

解 (a) M_2 从源端看入，输入电阻为 $\frac{1}{g_{m2}}$ ，而 M_1 为源简并放大器。则

$$\frac{v_X}{v_{in}} = -\frac{g_{m1}R_D}{1 + g_{m1} \cdot \frac{1}{g_{m2}}} = -\frac{g_m R_D}{2}$$

(b) M_1 为源极跟随器，则 M_1 源端电压即为 $v_{s1} = v_{in}$ ，而 M_2 为共栅放大器，则

$$\begin{aligned} \frac{v_Y}{v_{s1}} &= g_{m1}R_D \\ \therefore \frac{v_Y}{v_{in}} &= g_{m1}R_D \end{aligned}$$

(c)

$$\frac{v_X - v_Y}{v_{in}} = -\frac{3}{2}g_m R_D$$

这个增益是普通差分放大器增益的1.5倍。

10.70 Compute the common-mode rejection ratio of the stages illustrated in Fig. 10-89 and compare the results. For simplicity, neglect channel-length modulation in M_1 and M_2 but not in other transistors.

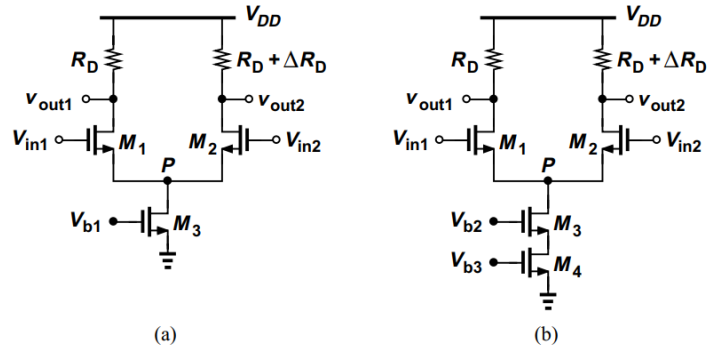


Figure 10-89

解

$$\text{CMRR} = 20 \log \left| \frac{A_{vd}}{A_{vc}} \right|$$

(a) 电路对称，可考虑半边电路。由交流小信号电路中 P 为虚地，则

$$A_{vd} = -g_{m1}R_D$$

考虑 A_{vc} 时，可将 M_3 视为 r_{o3} ，进而再半边电路中视为 $2r_{o3}$ ，则 M_1 为源简并放大器：

$$A_{vc} = \frac{-g_{m1}R_D}{1 + 2g_{m1}r_{o3}}$$

则

$$\text{CMRR} = 20 \log(1 + 2g_{m1}r_{o3})$$

(b) 同(a)， P 再交流小信号电路中仍未虚地，则

$$A_{vd} = -g_{m1}R_d$$

再考虑 A_{vc} ，将 M_4 视为 r_{o4} ，则 M_3 为源简并放大器，可视为电阻 $r = (1 + g_{m3}r_{o3})r_{o4} + r_{o3}$ 从而半边电路中可将其视为 $2r = 2[(1 + g_{m3}r_{o3})r_{o4} + r_{o3}]$ 此时 M_1 仍为源简并放大器：

$$\therefore A_{vc} = \frac{-g_{m1}R_D}{1 + 2g_{m1}[(1 + g_{m3}r_{o3})r_{o4} + r_{o3}]}$$

$$\therefore \text{CMRR} = 20 \log[1 + 2g_{m1}((1 + g_{m3}r_{o3})r_{o4} + r_{o3})]$$