Current Law $A^{\mathrm{T}}\boldsymbol{y} = \mathbf{0}$, we get $A^{\mathrm{T}}CA\boldsymbol{x} = \mathbf{0}$. This is *almost* the central equation for network flows. The only thing wrong is the zero on the right side! The network needs power from outside—a voltage source or a current source—to make something happen.

Note about signs In circuit theory we change from $A\boldsymbol{x}$ to $-A\boldsymbol{x}$. The flow is from higher potential to lower potential. There is (positive) current from node 1 to node 2 when $x_1 - x_2$ is positive—whereas $A\boldsymbol{x}$ was constructed to yield $x_2 - x_1$. The minus sign in physics and electrical engineering is a plus sign in mechanical engineering and economics. $A\boldsymbol{x}$ versus $-A\boldsymbol{x}$ is a general headache but unavoidable.

Note about applied mathematics Every new application has its own form of Ohm's Law. For springs it is Hooke's Law. The stress $\boldsymbol{y}$ is (elasticity C) times (stretching $A\boldsymbol{x}$). For heat conduction, $A\boldsymbol{x}$ is a temperature gradient. For oil flows it is a pressure gradient. For least squares regression in statistics (Chapter 12) C^{-1} is the covariance matrix.

My textbooks *Introduction to Applied Mathematics* and *Computational Science and Engineering* (Wellesley-Cambridge Press) are practically built on $A^{\mathrm{T}}CA$. This is the key to equilibrium in matrix equations and also in differential equations. Applied mathematics is more organized than it looks! *In new problems I have learned to watch for $A^{\mathrm{T}}CA$.*

Problem Set 10.1

Problems 1–7 and 8–14 are about the incidence matrices for these graphs.

1 Write down the 3 by 3 incidence matrix A for the triangle graph. The first row has -1 in column 1 and $+1$ in column 2. What vectors (x_1, x_2, x_3) are in its nullspace? How do you know that $(1, 0, 0)$ is not in its row space?

2 Write down A^{T} for the triangle graph. Find a vector $\boldsymbol{y}$ in its nullspace. The components of $\boldsymbol{y}$ are currents on the edges—how much current is going around the triangle?

3 Eliminate x_1 and x_2 from the third equation to find the echelon matrix U. What tree corresponds to the two nonzero rows of U?

$$\begin{aligned} -x_1 + x_2 &= b_1 \\ -x_1 + x_3 &= b_2 \\ -x_2 + x_3 &= b_3. \end{aligned}$$

4 Choose a vector (b_1, b_2, b_3) for which $A\boldsymbol{x} = \boldsymbol{b}$ can be solved, and another vector $\boldsymbol{b}$ that allows no solution. How are those $\boldsymbol{b}$'s related to $\boldsymbol{y} = (1, -1, 1)$?

5 Choose a vector (f_1, f_2, f_3) for which $A^{\mathrm{T}}\boldsymbol{y} = \boldsymbol{f}$ can be solved, and a vector $\boldsymbol{f}$ that allows no solution. How are those $\boldsymbol{f}$'s related to $\boldsymbol{x} = (1, 1, 1)$? The equation $A^{\mathrm{T}}\boldsymbol{y} = \boldsymbol{f}$ is Kirchhoff's _____ law.

6 Multiply matrices to find $A^{\mathrm{T}}A$. Choose a vector $\boldsymbol{f}$ for which $A^{\mathrm{T}}A\boldsymbol{x} = \boldsymbol{f}$ can be solved, and solve for $\boldsymbol{x}$. Put those potentials $\boldsymbol{x}$ and the currents $\boldsymbol{y} = -A\boldsymbol{x}$ and current sources $\boldsymbol{f}$ onto the triangle graph. Conductances are 1 because $C = I$.

7 With conductances $c_1 = 1$ and $c_2 = c_3 = 2$, multiply matrices to find $A^{\mathrm{T}}CA$. For $\boldsymbol{f} = (1, 0, -1)$ find a solution to $A^{\mathrm{T}}CA\boldsymbol{x} = \boldsymbol{f}$. Write the potentials $\boldsymbol{x}$ and currents $\boldsymbol{y} = -CA\boldsymbol{x}$ on the triangle graph, when the current source $\boldsymbol{f}$ goes into node 1 and out from node 3.

8 Write down the 5 by 4 incidence matrix A for the square graph with two loops. Find one solution to $A\boldsymbol{x} = \boldsymbol{0}$ and two solutions to $A^{\mathrm{T}}\boldsymbol{y} = \boldsymbol{0}$.

9 Find two requirements on the b's for the five differences $x_2 - x_1, x_3 - x_1, x_3 - x_2, x_4 - x_2, x_4 - x_3$ to equal b_1, b_2, b_3, b_4, b_5. You have found Kirchhoff's _____ law around the two _____ in the graph.

10 Reduce A to its echelon form U. The three nonzero rows give the incidence matrix for what graph? You found one tree in the square graph—find the other seven trees.

11 Multiply matrices to find $A^{\mathrm{T}}A$ and guess how its entries come from the graph:

(a) The diagonal of $A^{\mathrm{T}}A$ tells how many _____ into each node.

(b) The off-diagonals -1 or 0 tell which pairs of nodes are _____ .

12 Why is each statement true about $A^{\mathrm{T}}A$? *Answer for $A^{\mathrm{T}}A$ not A.*

(a) Its nullspace contains $(1, 1, 1, 1)$. Its rank is $n - 1$.

(b) It is positive semidefinite but not positive definite.

(c) Its four eigenvalues are real and their signs are _____ .

13 With conductances $c_1 = c_2 = 2$ and $c_3 = c_4 = c_5 = 3$, multiply the matrices $A^{\mathrm{T}}CA$. Find a solution to $A^{\mathrm{T}}CA\boldsymbol{x} = \boldsymbol{f} = (1, 0, 0, -1)$. Write these potentials $\boldsymbol{x}$ and currents $\boldsymbol{y} = -CA\boldsymbol{x}$ on the nodes and edges of the square graph.

14 The matrix $A^{\mathrm{T}}CA$ is not invertible. What vectors $\boldsymbol{x}$ are in its nullspace? Why does $A^{\mathrm{T}}CA\boldsymbol{x} = \boldsymbol{f}$ have a solution if and only if $f_1 + f_2 + f_3 + f_4 = 0$?

15 A connected graph with 7 nodes and 7 edges has how many loops?

16 For the graph with 4 nodes, 6 edges, and 3 loops, add a new node. If you connect it to one old node, Euler's formula becomes $(\quad) - (\quad) + (\quad) = 1$. If you connect it to two old nodes, Euler's formula becomes $(\quad) - (\quad) + (\quad) = 1$.

17 Suppose A is a 12 by 9 incidence matrix from a connected (but unknown) graph.

(a) How many columns of A are independent?

(b) What condition on $\boldsymbol{f}$ makes it possible to solve $A^{\mathrm{T}}\boldsymbol{y} = \boldsymbol{f}$?

(c) The diagonal entries of $A^{\mathrm{T}}A$ give the number of edges into each node. What is the sum of those diagonal entries?

18 Why does a complete graph with $n = 6$ nodes have $m = 15$ edges? A tree connecting 6 nodes has _____ edges.

Note The ***stoichiometric matrix*** in chemistry is an important "generalized" incidence matrix. Its entries show how much of each chemical species (each column) goes into each reaction (each row).